Homework: Resistance

- 1. Read 11.4
- Define and give an example the following two terms: superconductor, non-ohmic conductor
- 3. Pg. 465 #2, 3, 4
- 4. Pg. 467 #4-7

Electrical Resistance (11.4)

tric current,
ance's atoms

Resistors

- 2. Resistors are devices used in electric circuits to <u>safely</u> decrease the current by a certain amount.
 - They don't convert electrical energy into anything usable, but they do produce **heat** as a result.





Figure 1. Electrical resistors look small tubes or beads on the wire. Different sizes indicate different amounts of resistance.

Figure 2. Two circuit symbols representing resistor are shown. Even though they look different, they represent the same thing.

filament has less resistance than a hot filament.

Good conductors provide very little resistance to electrical current. The best conductors provide very little resistance - so little that it can be considered *negligible*.

Factors That Affect Resistance of a Wire

3. There are four major factors that will affect the resistance of a wire:

Factor	Description (complete by us	Description (complete by using the words higher or lower)			
Type of Material	Materials differ in their ator freely have	Materials differ in their atomic structure. Materials that allow electrons to flow freely have internal resistance. They are excellent conductors. Examples: copper, silver			
Length	The thicker the wire, the	the internal resistance it has.			
Diameter (thickness)	The longer the wire, the	the internal resistance.			
Temperature	The hotter the wire, the	the internal resistance.			
٥		0			
The type of material affects resistance. For example, a copper wire has less resistance compared with an iron wire of the same length and diameter.		A shorter wire has less resistance than a longer wire of the same diameter that is made from the same material.			
G		0			
		TO THE STATE OF TH			

Figure 11.25 Several factors affect the resistance of wires.

same length that is made from the same material.

Relating Current to Resistance and Voltage

Voltage, current, and resistance in a circuit are all related to each other. In general,


Homework: Ohm's Law

- 1. Ohm's Law practice problems
- 2. Pg. 464 #1-6
- 3. Pg. 467 #1-7

4.	When resistance is increased, current _	(increases/decreases).
5.	If voltage is increased, current	(increases/decreases).

Ohm's Law

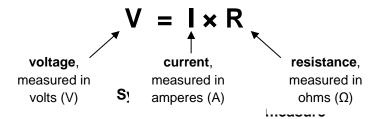Ohm's Law describes the relationship between three quantities: resistance, potential difference, and current. It is often expressed using the formula shown below.




Complete the chart:

Symbol	Variable/oltage	Unit of measure
	voltage current	
	current resistance	
	resistance	

6. The formula for Ohm's Law can be re-arranged to solve for *any* of the three variables, as long as the other two are known. Re-write Ohm's Law in its other two forms:

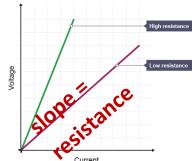- 7. a. Rising temperatures can lower a material's resistance. A resistor that obeys Ohm's Law will have a constant resistance, regardless of temperature. Such a resistor is called an ______ resistor.
 - b. Since R = V/I, a graph of voltage vs. current will always be a straight line for an ohmic resistor



Ohm's Law: Sample Problem

A technician is checking the circuits on a vehicle. The technician measures the current entering a component as 0.75 A. The potential difference across the component is 12 V. What is its **resistance**?

GIVEN: ANALYSIS & SOLUTION: STATEMENT:

REQUIRED:

Ohm's Law: Practice Problems

Text	Symbol	Factor	Factor (Sci. Not)
kilo	k	1 000	10 ³
hecto	h	100	10 ²
(none)	(none)	1	10 ⁰
deci	d	0.1	10-1
centi	С	0.01	10-2
milli	m	0.001	10 ⁻³

1. Find the unknown quantity. GRASS format is not required for these problems. If there are many decimals in your answer, report to **two** decimal places.

a)
$$I = 10 \text{ A}$$

 $R = 1500 \Omega$
 $V = ? V$

d)
$$I = ? A$$

 $R = 250 \Omega$
 $V = 175 V$

f)
$$I = 25 \text{ A}$$

 $R = 300 \Omega$
 $V = ? V$

2. Find the unknown quantity (CONVERT FIRST to the unit with no prefix)

b)
$$I = 25 \text{ mA} =$$
_____ A $R = ? \Omega$ $V = 110 \text{ V}$

3. How much resistance does a light bulb create if it has a current of 25 mA around it in a 9 V circuit? GIVEN: ANALYSIS & SOLUTION: STATEMENT: REQUIRED: 4. A heating coil offers a resistance of 2.5 kΩ. What **voltage** is required so that 1.5 A of current pass through it? 5. An electric toy has a resistance of 120 Ω , and requires a current of 0.050 A to work properly. **How many 1.5** V cells does the toy require? 6. The human body offers a very small amount of resistance (let's say 1 m Ω for argument). If a lightning bolt (said to have 1.21 GV, or 1 210 000 000 V of potential according to a famous movie called Back to the Future released in 1984), hits you, how much current is flowing through your body? Express your answer in amperes, and in gigamperes (if you can!).

WORD PROBLEMS Use GRASS format for each of these word problems.